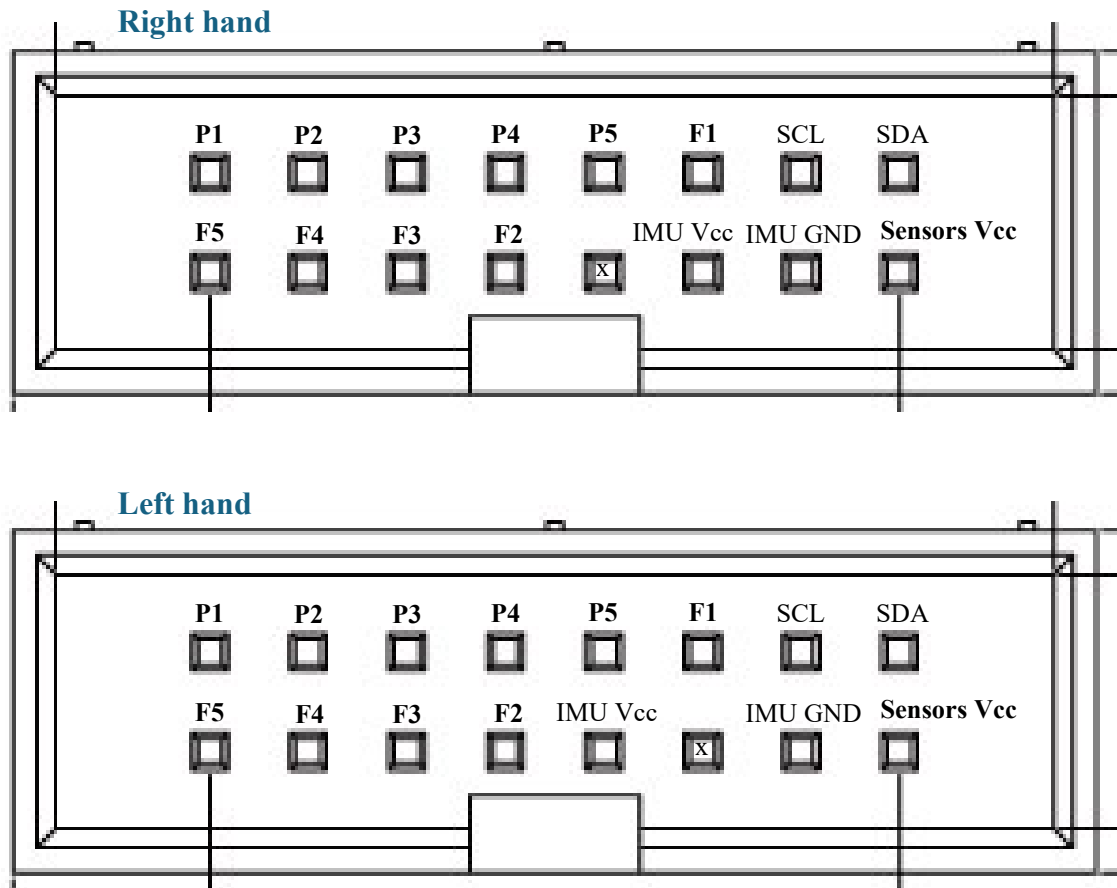


a) Glove pins mapping:



b) Circuit design:

- Connected the right-hand glove onto a breadboard along with pulldown resistors and capacitors FSR sensors: 10k resistor and 10nF capacitor. 47k resistor and 100nF capacitor for flex sensors
- Connected a CD4067 MUX and an M5Stick CPlus 1.1 as follows:

Mux pin	Connected to	Purpose
Vdd	3.3V	Power
GND	GND	Ground
EN	GND	Active-low enable pin
SIG	M5: G36	"Analog Out" sent to the M5
S0	M5: G26	Selection Bit 0
S1	M5: G32	Selection Bit 1
S2	M5: G33	Selection Bit 2
S3	M5: G0	Selection Bit 3
C0	Press 1	Thumb FSR sensor
C1	Press 2	Index FSR sensor
C2	Press 3	Middle FSR sensor

C3	Press 4	Ring FSR sensor
C4	Press 5	Pinky FSR sensor
C5	Flex 1	Thumb Flex sensor
C6	Flex 2	Index Flex sensor
C7	Flex 3	Middle Flex sensor
C8	Flex 4	Ring Flex sensor
C9	Flex 5	Pinky Flex sensor

- Note that the IMU connections of the glove are left unused given that the built-in IMU in M5Stick will be used instead